

# COMBINATIONL LOGIC CIRCUITS

# OBJECTIVE

- To design, construct, and test four combinational logic circuits. The first two circuits are to be constructed with NAND gates, the third with XOR gates, and the fourth with a decoder and NAND gates.

# CIRCUIT 1

To design a combinational circuit with four inputs— A, B, C, and D —and one output, F . F is to be equal to 1 when A = 1, provided that B = 0, or when B = 1, provided that either C or D is also equal to 1. Otherwise, the output is to be equal to 0.

# Truth Table

A	B	C	D	F
0	0	0	0	<b>0</b>
0	0	0	1	<b>0</b>
0	0	1	0	<b>0</b>
0	0	1	1	<b>0</b>
0	1	0	0	<b>0</b>
0	1	0	1	<b>1</b>
0	1	1	0	<b>1</b>
0	1	1	1	<b>1</b>

A	B	C	D	F
1	0	0	0	<b>1</b>
1	0	0	1	<b>1</b>
1	0	1	0	<b>1</b>
1	0	1	1	<b>1</b>
1	1	0	0	<b>0</b>
1	1	0	1	<b>1</b>
1	1	1	0	<b>1</b>
1	1	1	1	<b>1</b>

$$F = AB' + BC + BD$$

# Function using NAND gates



$$F = AB' + BC + BD$$

$$F' = (AB' + BC + BD)'$$


$$(F')' = [(AB')'(BC)'(BD)']'$$

$$F = [(AB')'(BC)'(BD)']'$$

# Logic Diagram in LTSpice

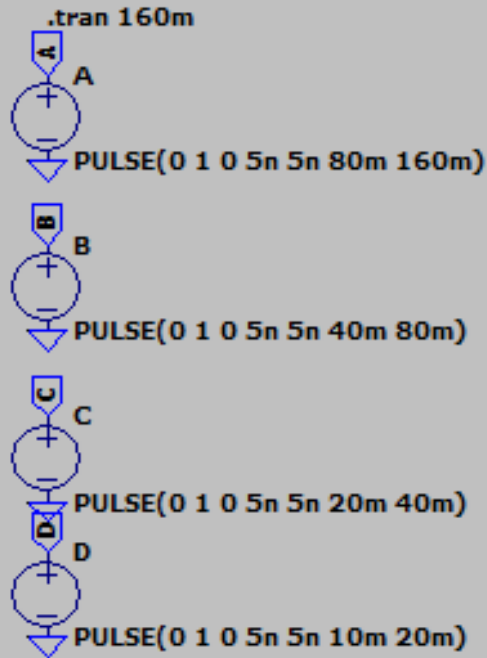 

# Output from LTSpice

 

# CIRCUIT 2 (Majority Logic)

A majority logic is a digital circuit whose output is equal to 1 if the majority of the inputs are 1's. The output is 0 otherwise. Design and test a three-input majority circuit using NAND gates with a minimum number of ICs.



# Truth Table

A	B	C	F
0	0	0	<b>0</b>
0	0	1	<b>0</b>
0	1	0	<b>0</b>
0	1	1	<b>1</b>
1	0	0	<b>0</b>
1	0	1	<b>1</b>
1	1	0	<b>1</b>
1	1	1	<b>1</b>

$$F = AB + BC + CA$$

# Function using NAND gates



$$F = AB + BC + CA$$

$$F' = (AB + BC + CA)'$$


$$(F')' = [(AB)'(BC)'(CA)']'$$

$$F = [(AB)'(BC)'(CA)']'$$

# Logic Diagram in LTSpice

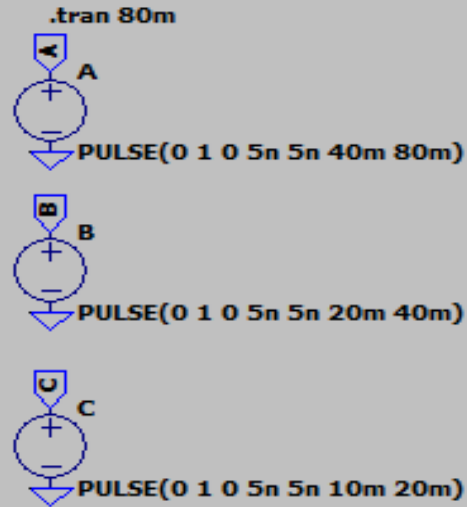 

# Output from LTSpice

 

# CIRCUIT 3(PARITY GENERATOR)

Design, construct, and test a circuit that generates an even parity bit from four message bits. Use XOR gates. Adding one more XOR gate, expand the circuit so that it generates an odd parity bit also.

# Truth Table

A	B	C	D	Even	Odd
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	1	0

A	B	C	D	Even	Odd
1	0	0	0	1	0
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	0	1

# Output Function



$$\text{EVEN} = A \oplus B \oplus C \oplus D$$

$$\text{EVEN} = (A \oplus B) \oplus (C \oplus D)$$

$$\text{ODD} = \text{EVEN}'$$

$$\text{ODD} = \text{EVEN} \oplus 1$$


# Logic Diagram in LTSpice

  



For Even Parity Checker



# Output from LTSpice

 


# Logic Diagram in LTSpice

  

For Odd Parity Checker

# Output from LTSpice

 

# CIRCUIT 4(DECODER IMPLEMENTATION)

A combinational circuit has three inputs— x, y, and z —and three outputs— F1, F2, and F3. The simplified Boolean functions for the circuit are

$$F1 = xz + xyz$$

$$F2 = xy + xyz$$

$$F3 = xy + xyz$$

Implement and test the combinational circuit, using a 74155 decoder IC and external NAND gates,

# Truth Table

X	Y	Z	F1	F2	F3
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	0
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	1

$$F1 = XZ + X'Y'Z'$$

$$F2 = X'Y + XY'Z'$$

$$F3 = XY + X'Y'Z$$

# Functions using NAND Gates

$$F1 = XZ + X'Y'Z'$$

$$F1 = XZ(Y + Y') + X'Y'Z'$$

$$F1 = XYZ + XY'Z + X'Y'Z'$$

$$(F1)' = [(XYZ)'(XY'Z)'(X'Y'Z)']'$$

$$F1 = [(XYZ)'(XY'Z)'(X'Y'Z)']'$$

$$F2 = X'Y + XY'Z'$$

$$F2 = X'Y(Z + Z') + XY'Z'$$

$$F2 = X'YZ + X'YZ' + XY'Z'$$

$$(F2)' = [(X'YZ)'(X'YZ')'(XY'Z)']'$$

$$F2 = [(X'YZ)'(X'YZ')'(XY'Z)']'$$

$$F3 = XY + X'Y'Z$$


$$F3 = XY(Z + Z') + X'Y'Z$$

$$F3 = XYZ + XYZ' + X'Y'Z$$


$$(F3)' = [(XYZ)'(XYZ')'(X'Y'Z)']'$$

$$F3 = [(XYZ)'(XYZ')'(X'Y'Z)']'$$

# Logic Diagram in LTSpice

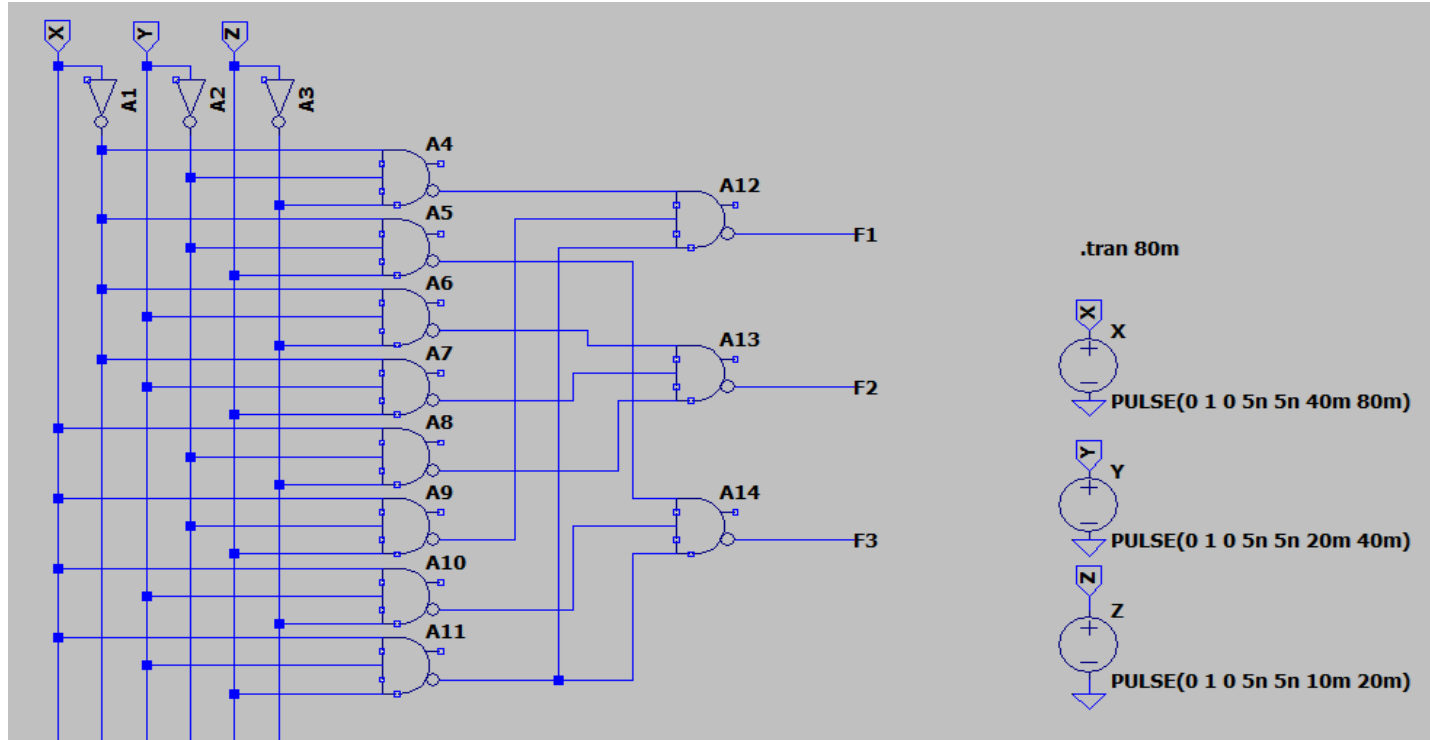


# Output from LTSpice

 

For F1




# Output from LTSpice

 

For F2


# Output from LTSpice

 

For F3
 
# Spikes in the Output

The waveform shown by LTspice is not exactly ideal. We set the voltage to instantly turn from 0 to 1V, but the program executes this by ramping up in a short amount of time. This creates spikes in the output waveform.



## Zooming the spike

The diagram shows one such transition and how it changes the output waveform.

